

**VIT**<sup>®</sup>**Vellore Institute of Technology**  
(Deemed to be University under section 3 of UGC Act, 1956)

<b>Reg.No</b>	19BEC0358		
<b>Student Name</b>	ARPIT PATAWAT		
<b>Course Code</b>	ECE3002	<b>Slot &amp; Semester</b>	L43+L44 WINTER -- 2021-22
<b>Course Name</b>	VLSI system design		
<b>Program Title</b>	Lab Assignment 2		
<b>Faculty</b>	Dr. Ragunath G		



**School of Electronics Engineering ,VIT, Vellore**

- 
1. Design a 2 input MUX using Pass Transistor Logic (using NMOS)
  2. Design a 2 input MUX using Transmission Gate Logic.


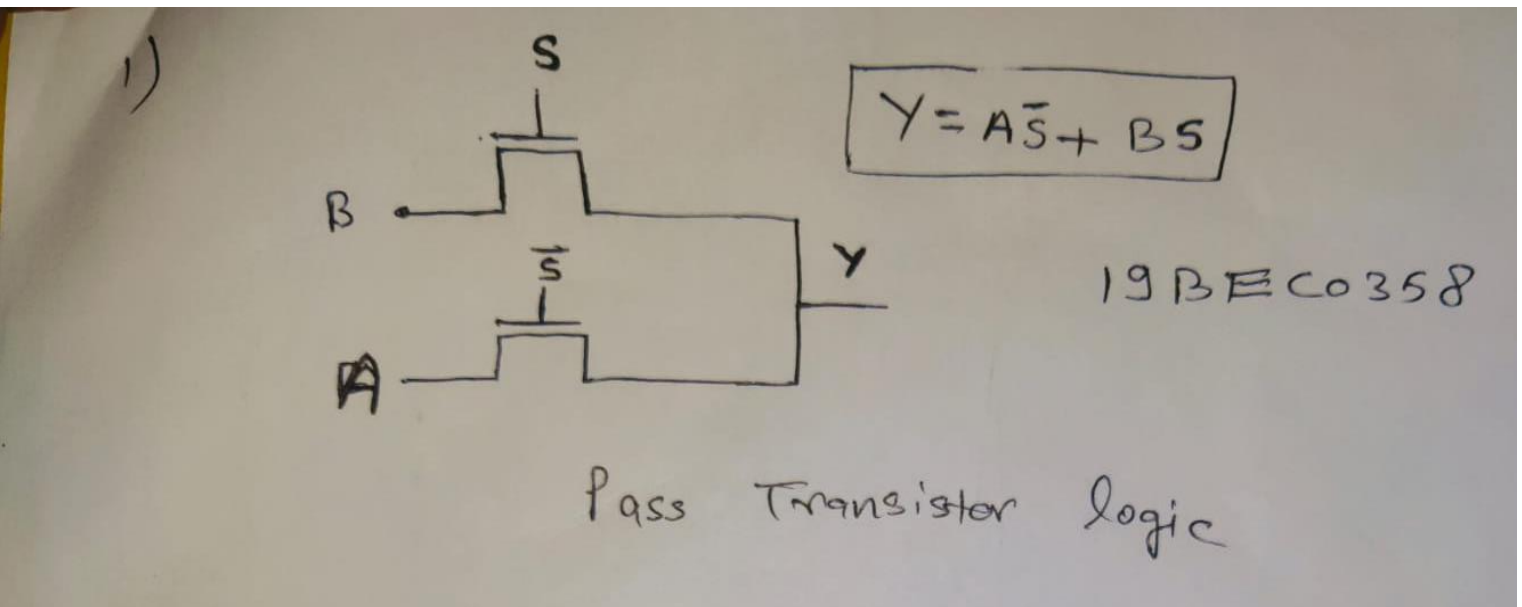
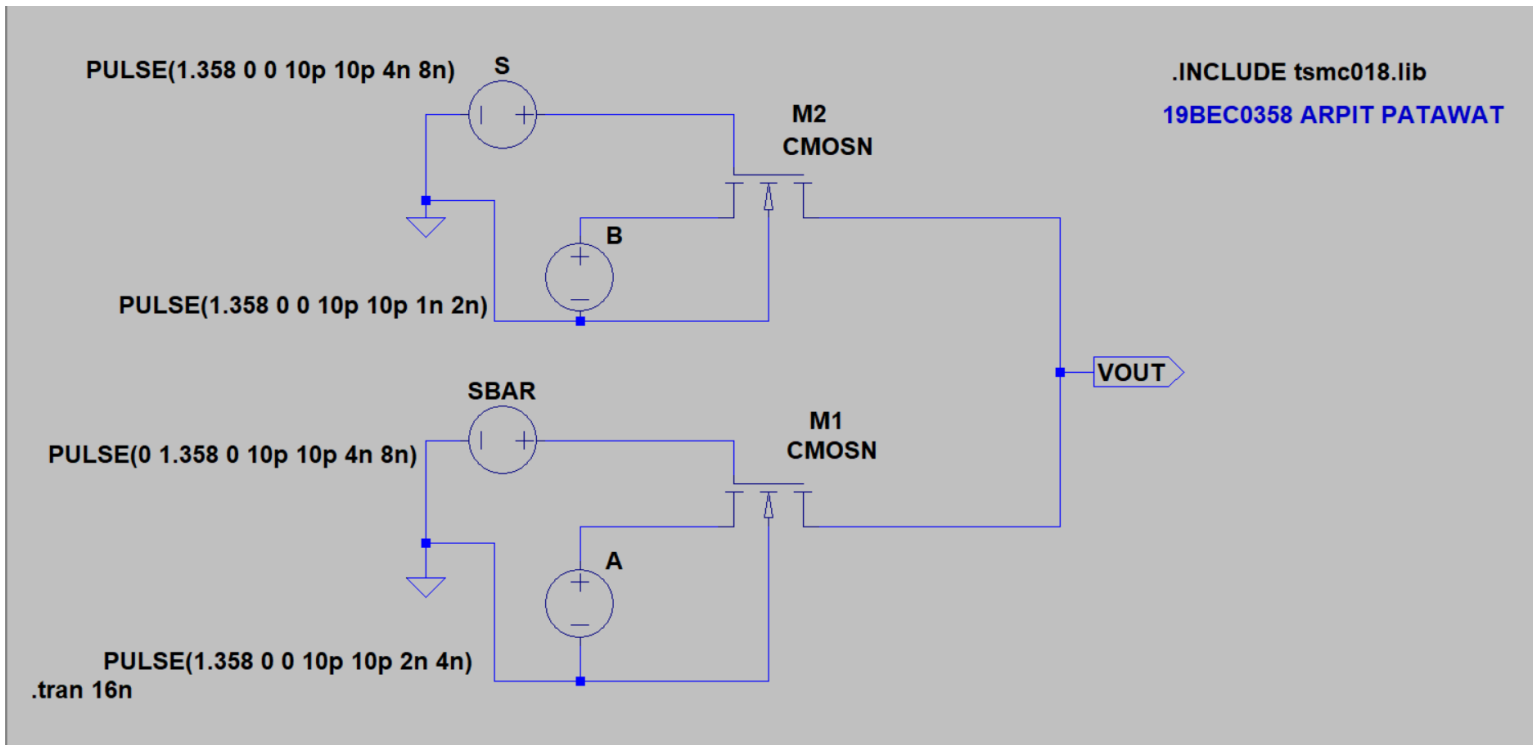
1).

Aim → to design MUX using pass transistor logic

Circuit Diagram → Width = length = 180 nm



## Simulation →

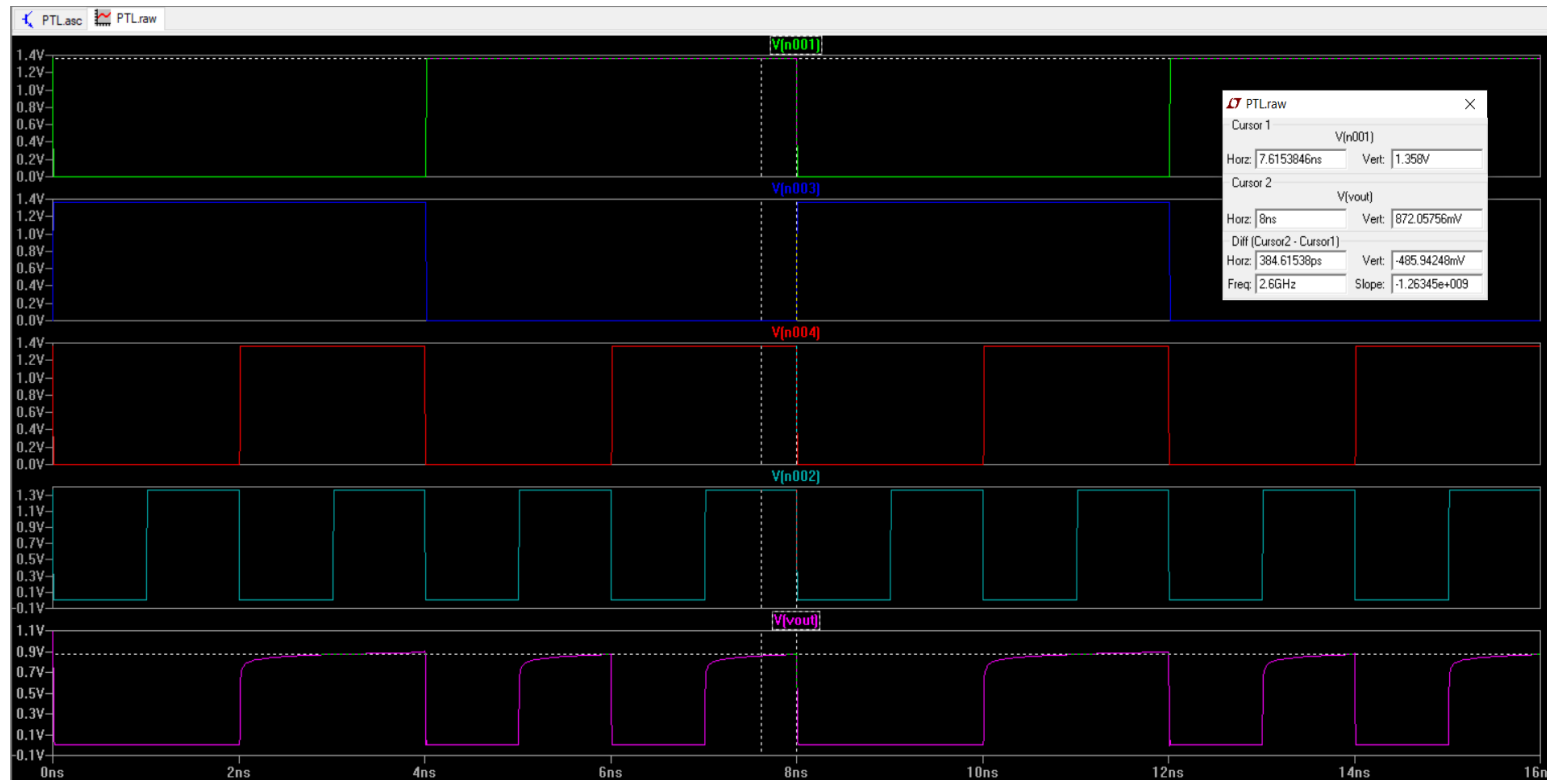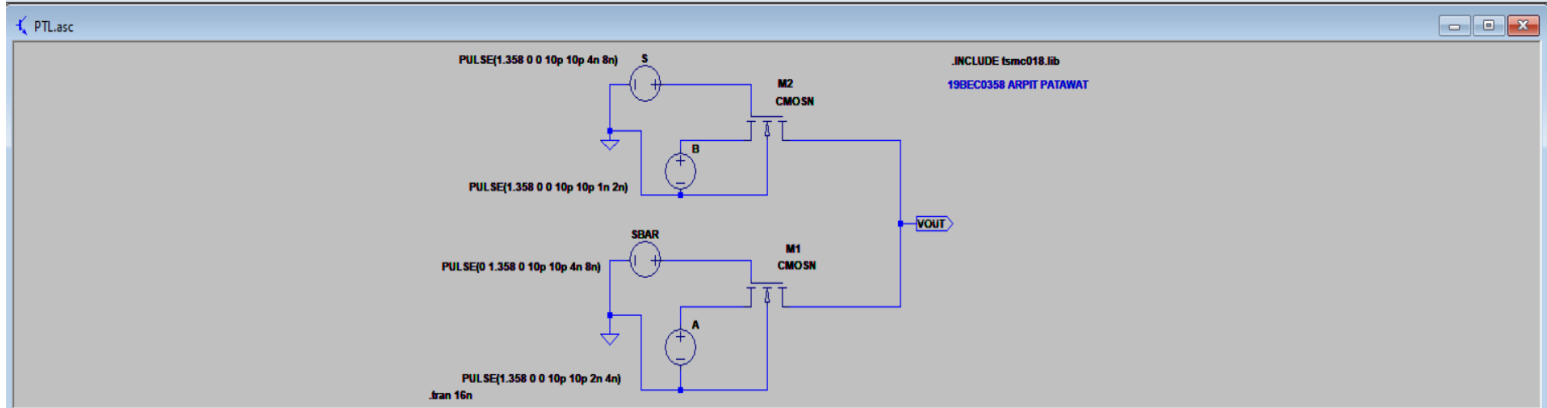 


## Result →


Here we can see 5 waves, which are Select line, compliment of select line, Input A, Input B and finally the Output B respectively. When Select line is 0 then output is A and when select line is 1 then output is B. since we are using pass transistor logic so we can expect degraded 1 output which can be seen as input is 1.358V(VDD) but output is 0.872V which is near to  $V_{DD} - V_{th}$  or  $(1.358 - 0.45)$  V

2.


Aim → to design MUX using Transistor gate logic


Circuit Diagram →

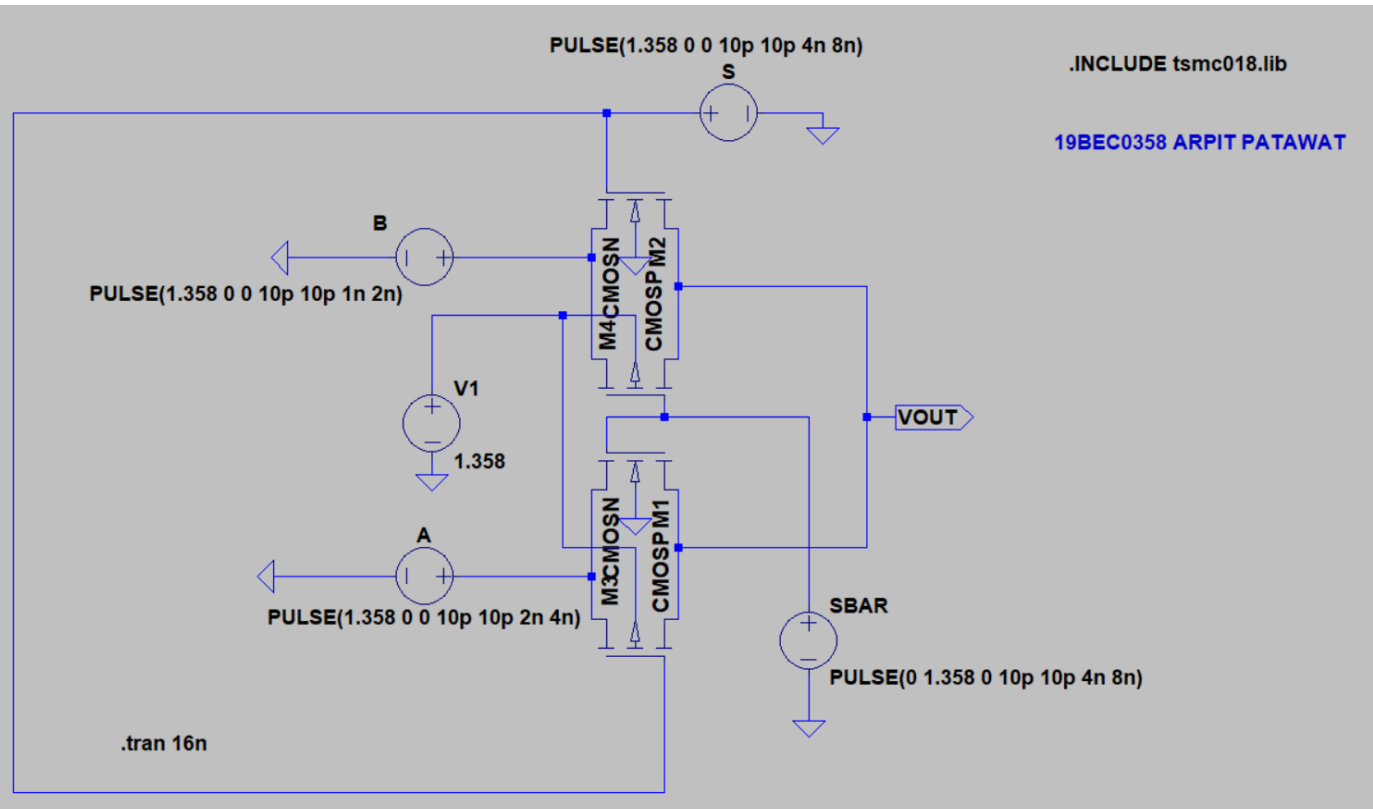

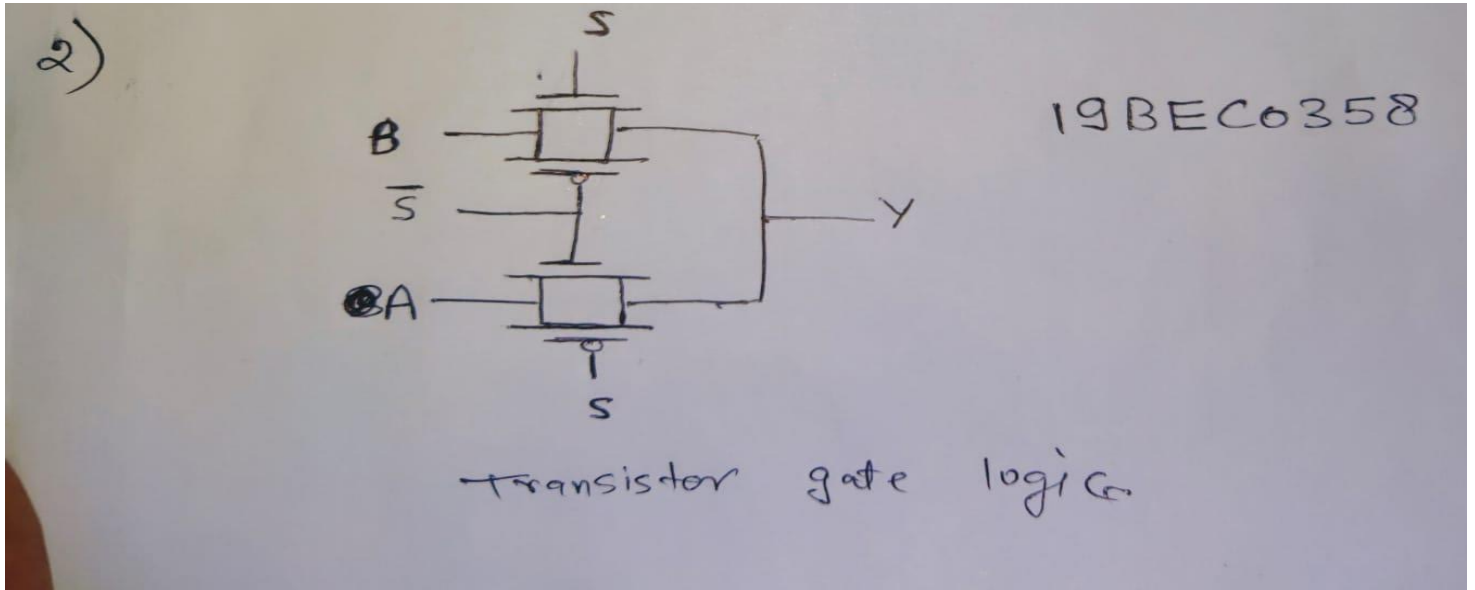

Simulation →

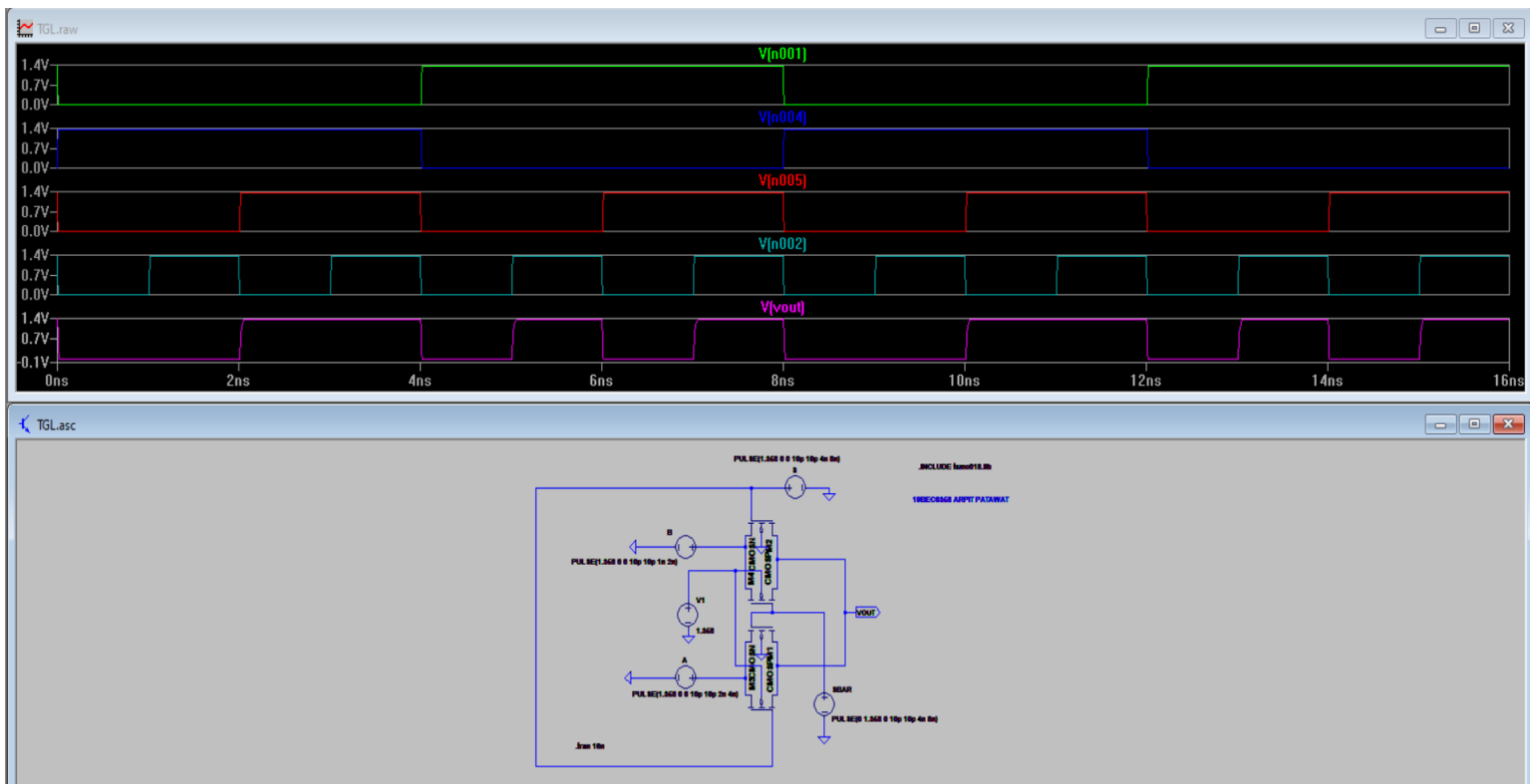

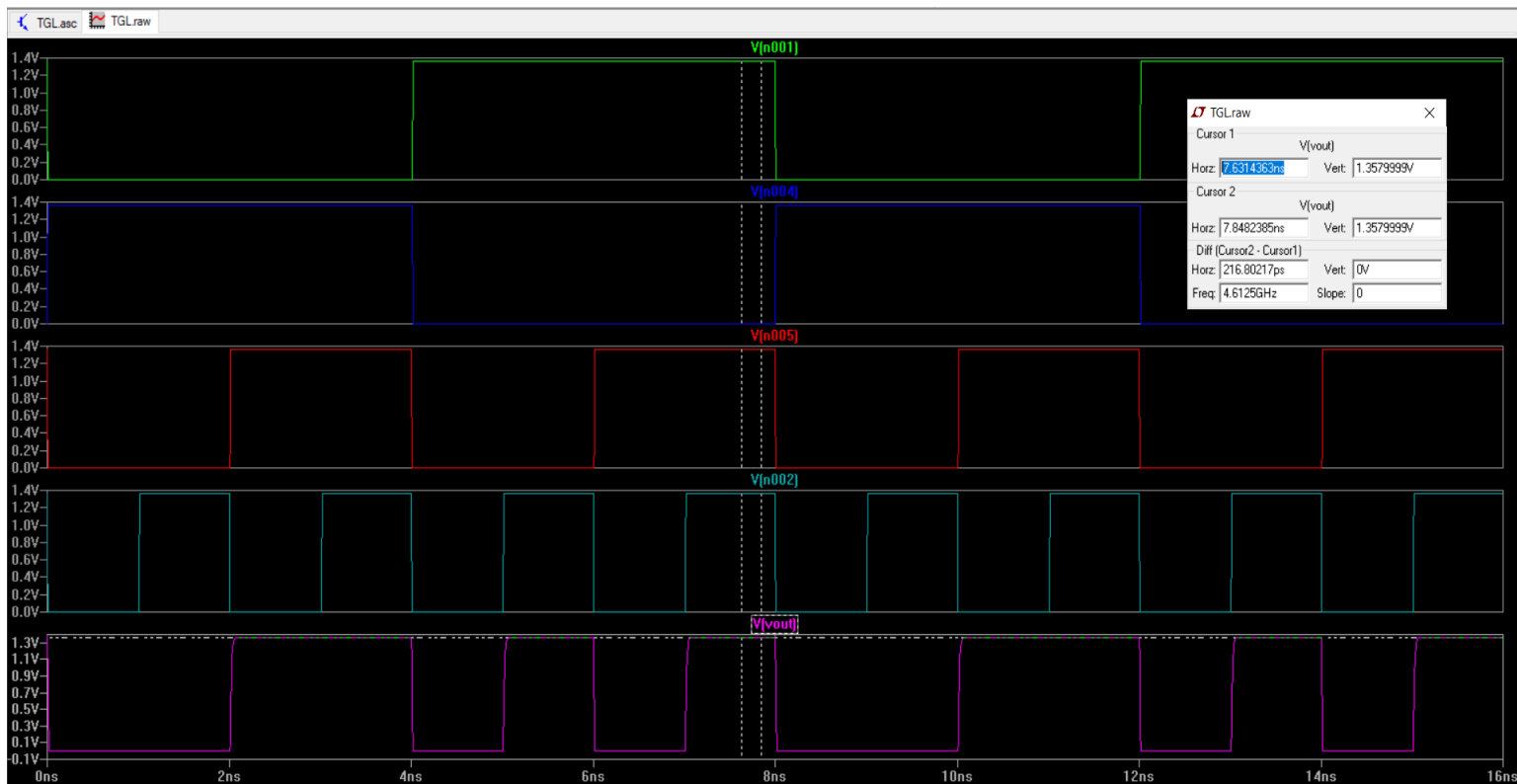

## Result →

Here we can see 5 waves, which are Select line, compliment of select line, Input A, Input B and finally the Output B respectively. When Select line is 0 then output is A and when select line is 1 then output is B. since we are using transistor gate logic so we can expect correct output VDD (1.358V).

-----XXXXX-----