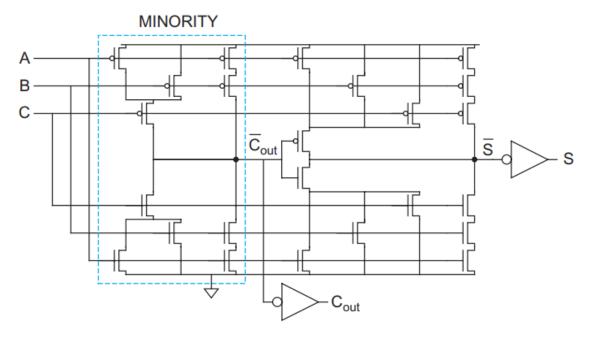



Reg.No	19BEC0358				
Student Name	ARPIT PATAWAT				
Course Code	ECE3002	Slot & Semester	L43+L44		
			WINTER 2021-22		
Course Name	VLSI system design				
Program Title	Lab Assignment 4				
Faculty	Dr. Ragunath G				


School of Electronics Engineering ,VIT, Vellore

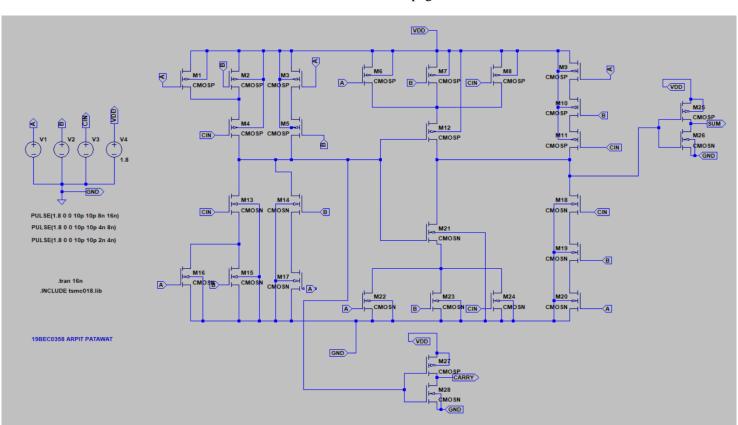- 1. Design a Full adder in Static CMOS logic with proper sizing of transistors.
- 2. Verify with inputs and outputs.
- 3. Create a symbol for the full adder.
- 4. Design a Four-bit ripple carry adder using symbol of the full adders
- 5. Verify with inputs and outputs




Note: - Circuit referred from book CMOS VLSI DESIGN page -432



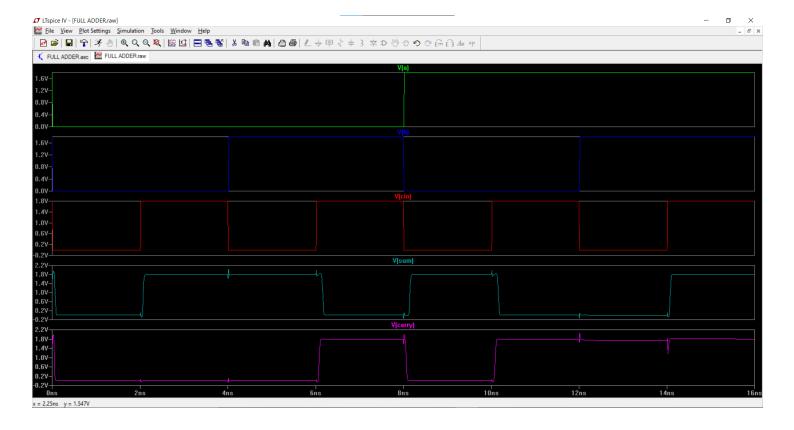



TRUTH TABLE →


INPUTS			OUTPUTS	
A	В	CIN	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

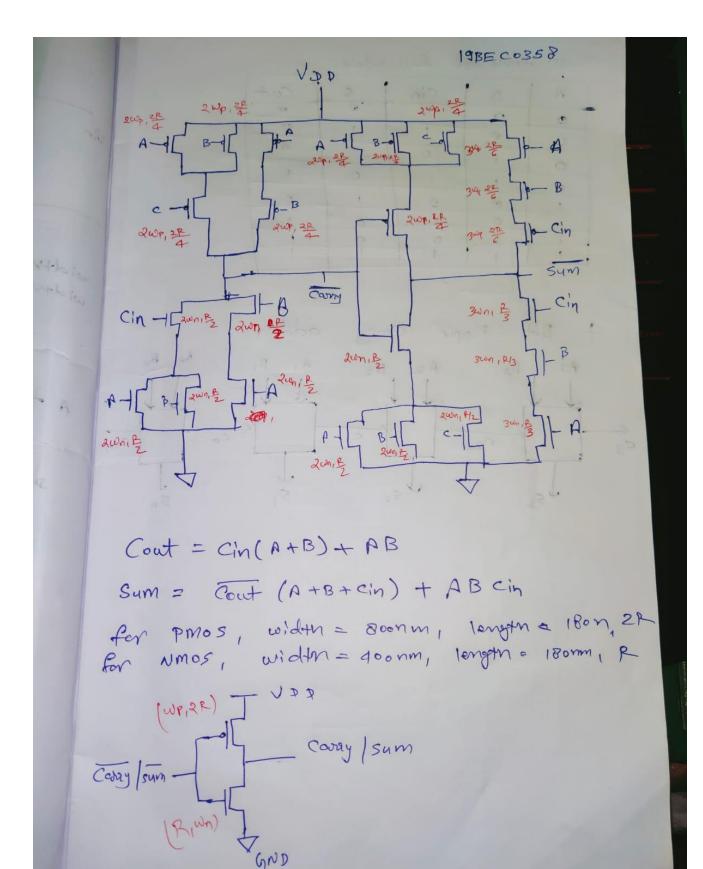


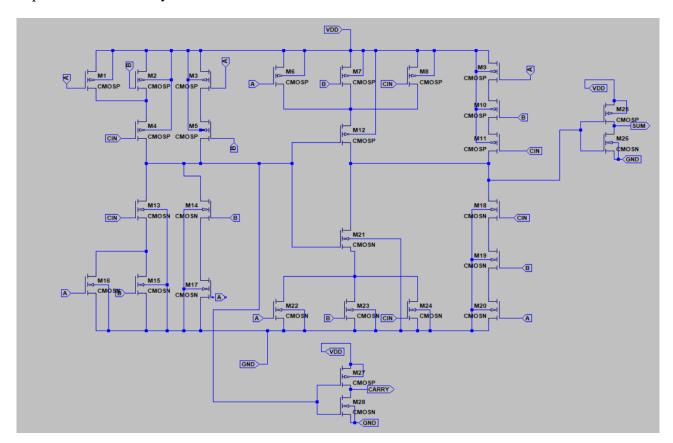
Symbol Creation → while creating full adder, before adding all the voltage sources, I copied the circuit for symbol creation into a new file.



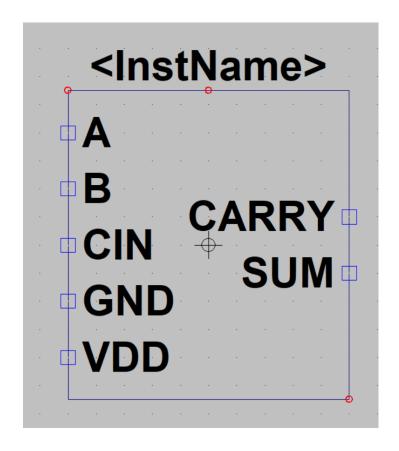

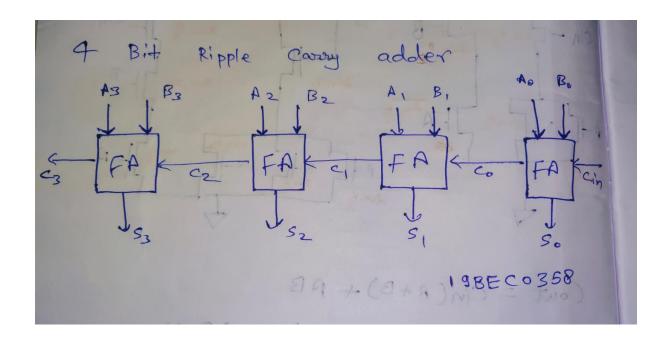

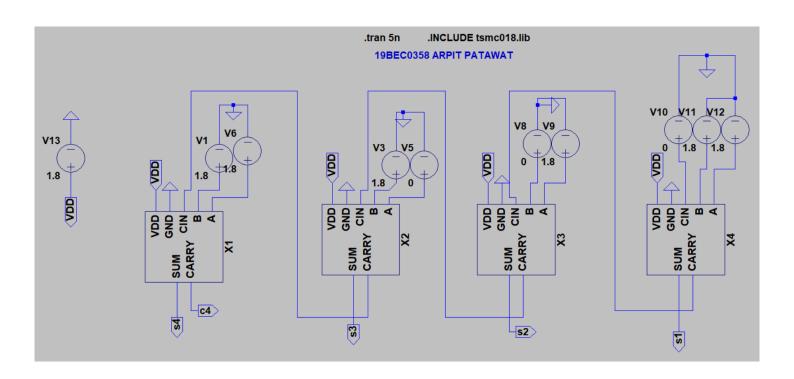

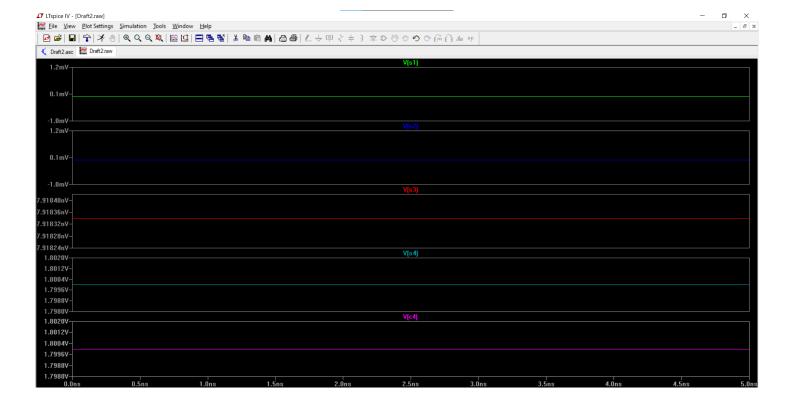

Result \rightarrow Here, in this task we designed a full adder in static CMOS design with proper sizing of transistors and created symbol for the same and verified it with inputs and outputs. Also, we designed a four-bit ripple carry adder using symbol using the full adders and verified with inputs and outputs. At page 6 I took an example of addition of 2 numbers and the same output can be seen at the graph here.

